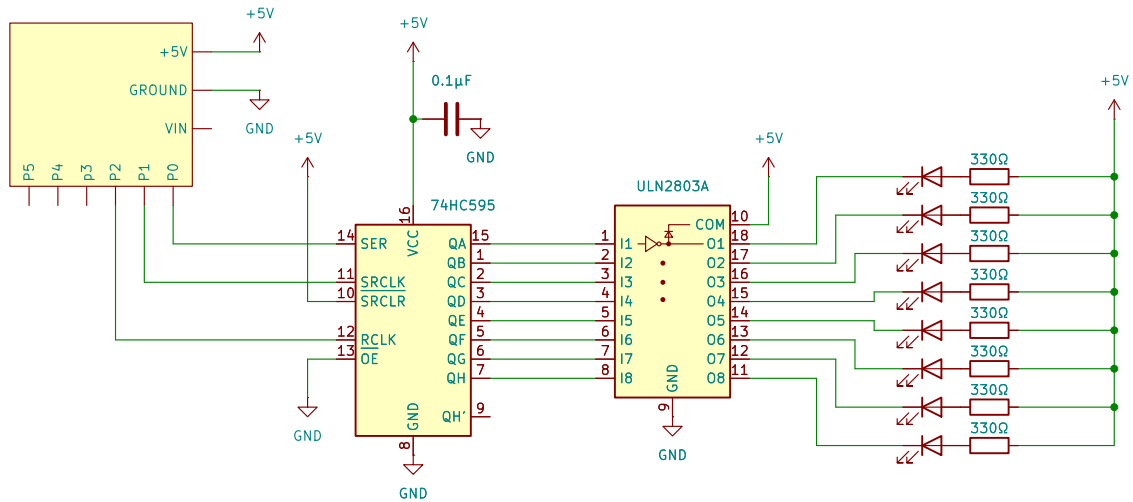


Project Colin Digispark ATTiny LED chaser light



I have added a 0.1μF decoupling capacitor between the 74HC595's VCC pin and GND. Its job is to smooth out the power supply to the sensitive shift register chip.

